

# General Dynamic Gyrator Models for Transient Analysis of IPT

Chun T. Rim  
GIST



+82-62-715-5325  
ctrim(at)gist.ac.kr  
<http://tesla.gist.ac.kr/>

# Contents

## I. Introduction

## II. Dynamic Phasor-based Gyrator Model of IPT

### A. Dynamic Gyrator

### B. Dynamic Phasor Circuit of an IPT

### C. Dynamic Gyrator-based IPT Analysis

## III. Verifications by Simulation

## IV. Experimental Verifications


## V. Concluding Remark

---

# I. Introduction

# Principle of Inductive Power Transfer (IPT)

□ IPT is a sort of “coupled inductors”

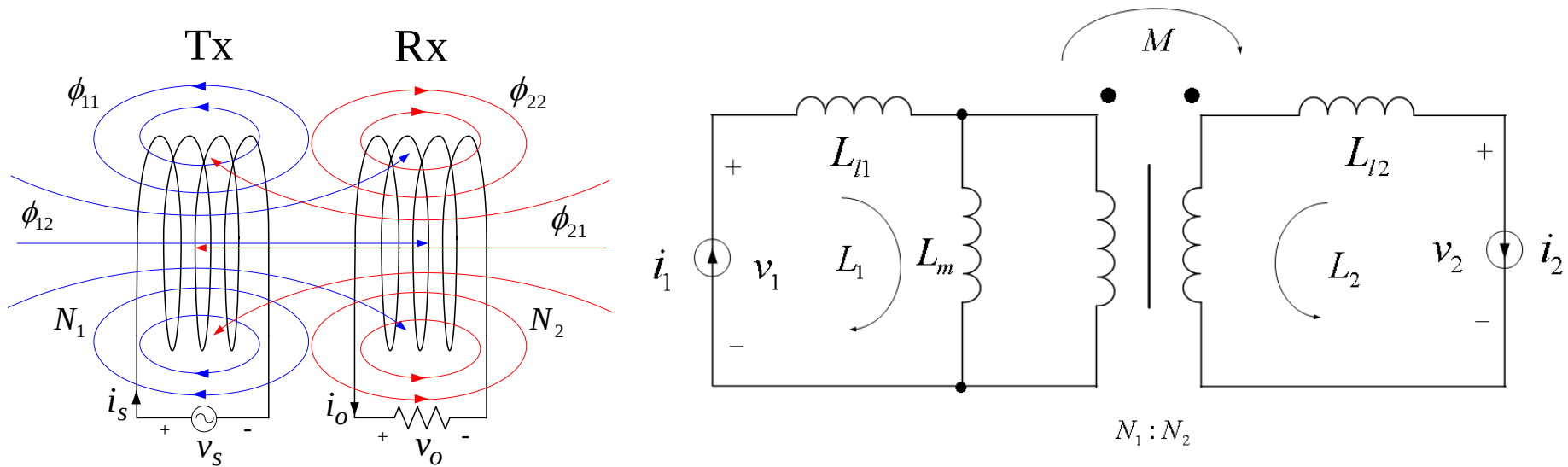


$$v_1 = N_1(\dot{\phi}_{11} + \dot{\phi}_{12} - \dot{\phi}_{21}) = L_{l1} \dot{i}_1 + (L_{12} \dot{i}_1 - L_{21} \dot{i}_2 / n)$$

$$v_2 = -N_2(\dot{\phi}_{22} + \dot{\phi}_{21} - \dot{\phi}_{12}) = -L_{l2} \dot{i}_2 - (L_{21} \dot{i}_2 - n L_{12} \dot{i}_1)$$

# Principle of Inductive Power Transfer (IPT)

## □ M-model & T-model

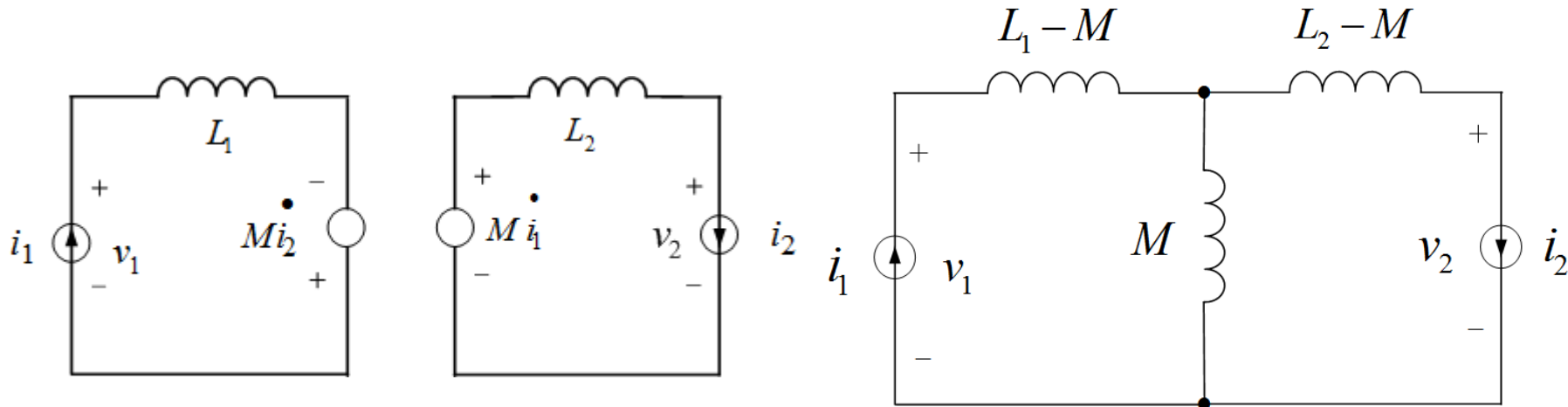


$$v_1 = L_{l1} \dot{i}_1 + L_m (\dot{i}_1 - n \dot{i}_2) = (L_{l1} + L_m) \dot{i}_1 - n L_m \dot{i}_2 \equiv L_1 \dot{i}_1 - M \dot{i}_2$$


$$v_2 = (n L_m \dot{i}_1 - n^2 L_m \dot{i}_2) - L_{l2} \dot{i}_2 = n L_m \dot{i}_1 - (n^2 L_m + L_{l2}) \dot{i}_2 \equiv M \dot{i}_1 - L_2 \dot{i}_2$$
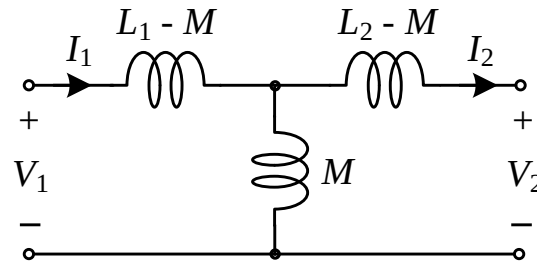
# Static Gyrator Model for the Steady State IPT


□ Static G-Model:  $I_1 = \frac{-1}{jX_0} \times V_2 \quad I_2 = \frac{1}{jX_0} \times V_1$



(a) Equivalent T-model of IPT

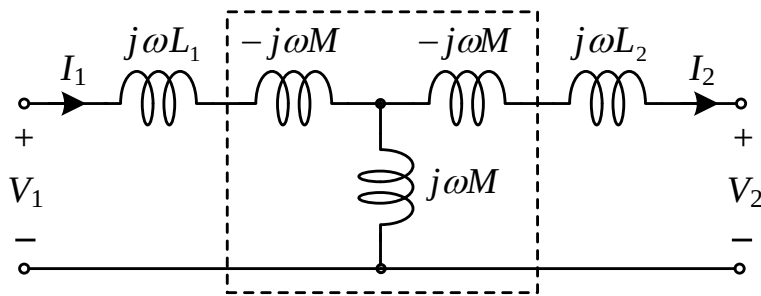

(b) Equivalent circuit of (a)

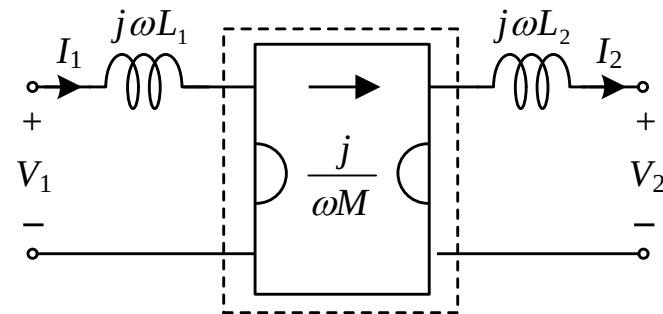


(c) Static gyrator-model

[34] Y. H. Sohn, B. H. Choi, G. -H. Cho and C. T. Rim, "Gyrator-Based Analysis of Resonant Circuits in Inductive Power Transfer Systems," IEEE Transactions on Power Electronics, vol. 31, no. 10, pp. 6824-6843, Oct. 2016.

# Static Gyrator Model for the Steady State IPT

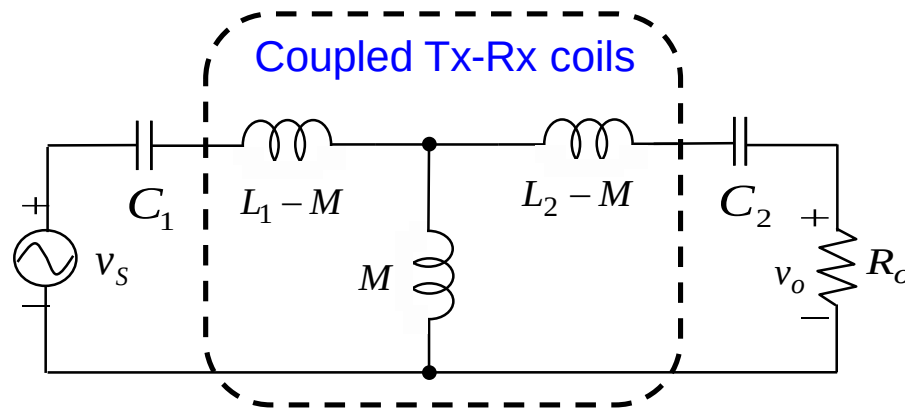
## □ Voltage source S-S IPT example (tuned in the steady state)




$$V_o = I_o R_o = \frac{jV_s R_o}{\omega_s M}$$

$$\Rightarrow I_s = \frac{-jV_o}{\omega_s M} = \frac{-j}{\omega_s M} \frac{jV_s R_o}{\omega_s M} = \frac{V_s R_o}{(\omega_s M)^2}$$
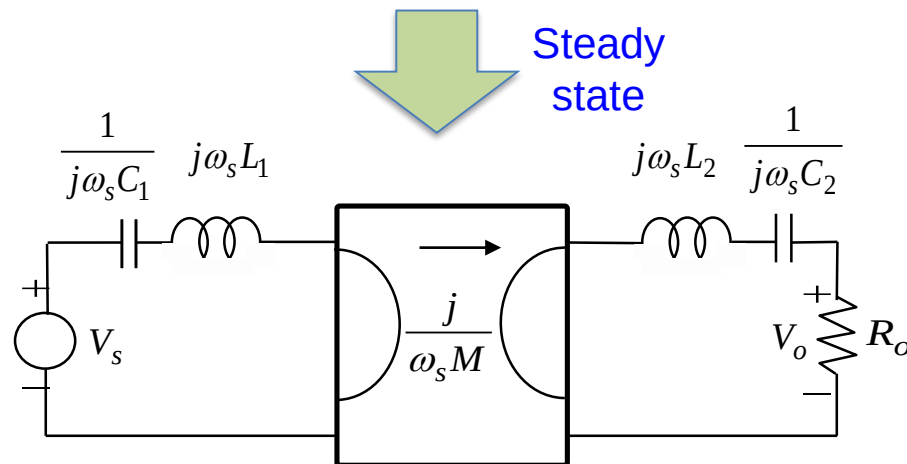
$$\Rightarrow P_s = P_o = V_s I_s = \frac{V_s^2 R_o}{(\omega_s M)^2} = \frac{V_s^2}{R_{eff}}, \quad \because R_{eff} \equiv \frac{(\omega_s M)^2}{R_o}$$



Tuned case

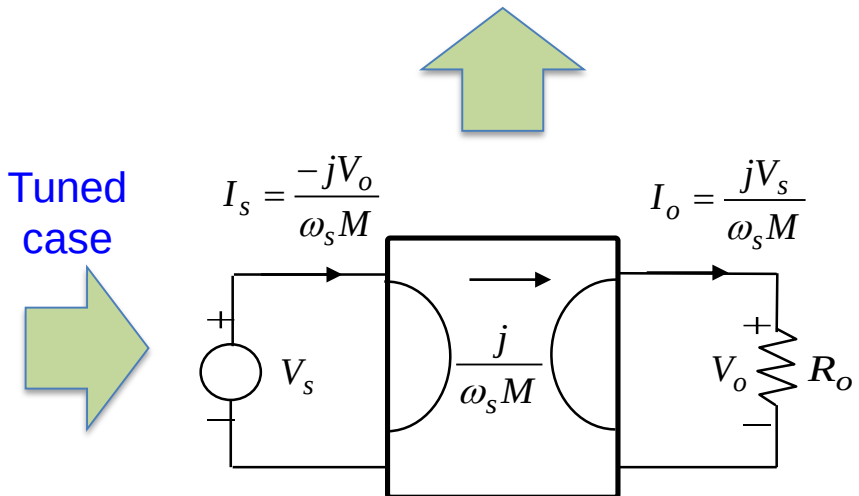


---

## II. Dynamic Phasor-based Gyrator Model of IPT




# Dynamic Gyrator Model for the Transient State IPT
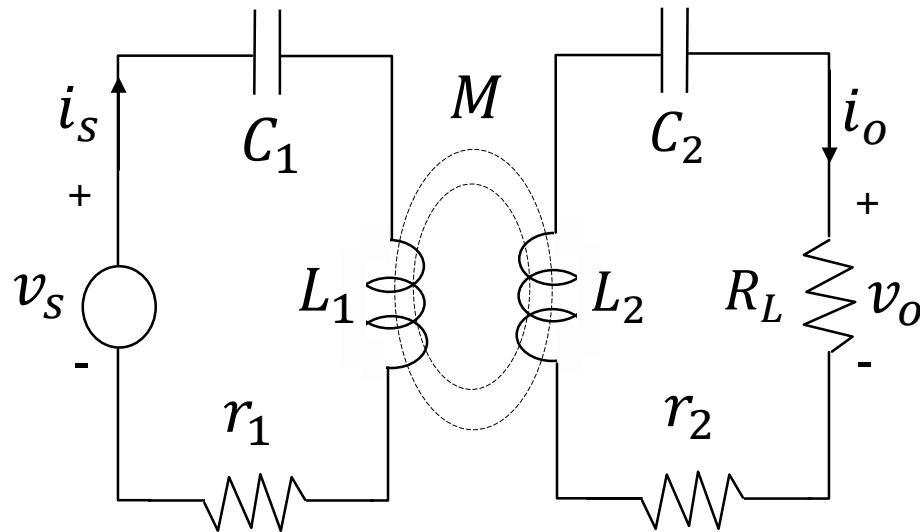
## □ Proposed S-S IPT with internal resistances



# Dynamic Gyrator Model for the Transient State IPT
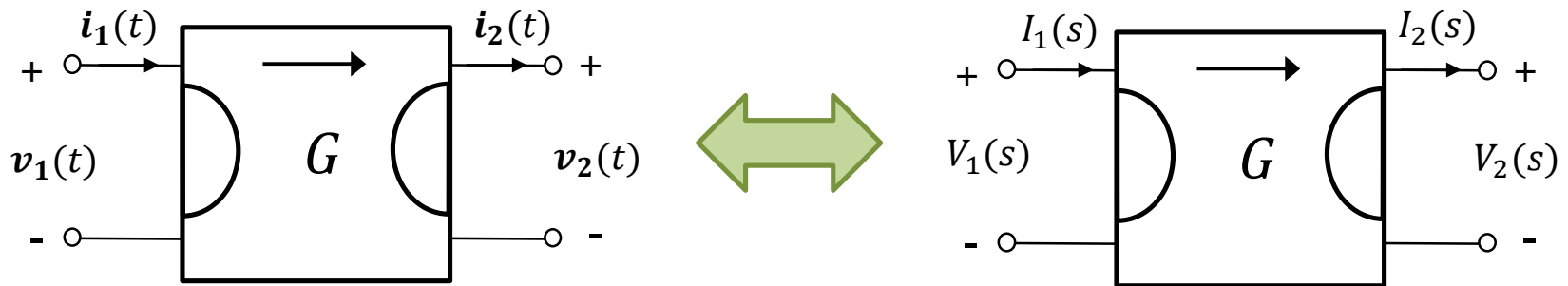
## □ Proposed dynamic gyrators (time domain vs. frequency domain)



$$i_2(t) = \mathbf{G}v_1(t)$$


$$i_1(t) = \mathbf{G}^*v_2(t)$$

$$I_2(s) = \mathbf{G}V_1(s)$$

$$I_1(s) = \mathbf{G}^*V_2(s)$$

# Dynamic Gyrator Model for the Transient State IPT
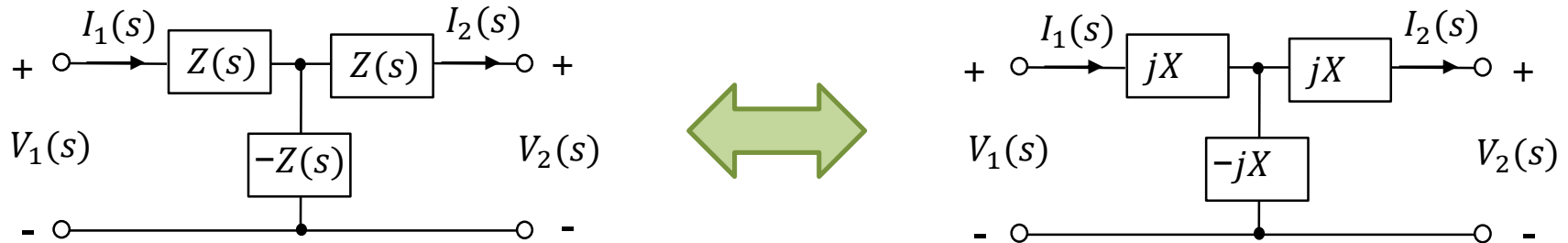
## □ Dynamic T-Model: Conditions for Imaginary gyrator




$$V_1(s) = -Z(s)\{I_1(s) - I_2(s)\} + Z(s)I_1(s) = Z(s)I_2(s)$$

$$V_2(s) = -Z(s)\{I_1(s) - I_2(s)\} + Z(s)\{-I_2(s)\} = Z(s)I_1(s)$$

+

$$I_2(s) = \mathbf{G}V_1(s)$$

$$I_1(s) = \mathbf{G}^*V_2(s)$$

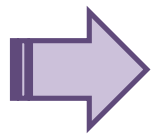


$$\mathbf{G} = 1/Z(s), \quad \mathbf{G}^* = 1/Z^*(s) = -1/Z(s)$$

$$Z^*(s) = -Z(s) \rightarrow \text{Re}\{Z(s)\} = 0 \rightarrow Z(s) = jX$$
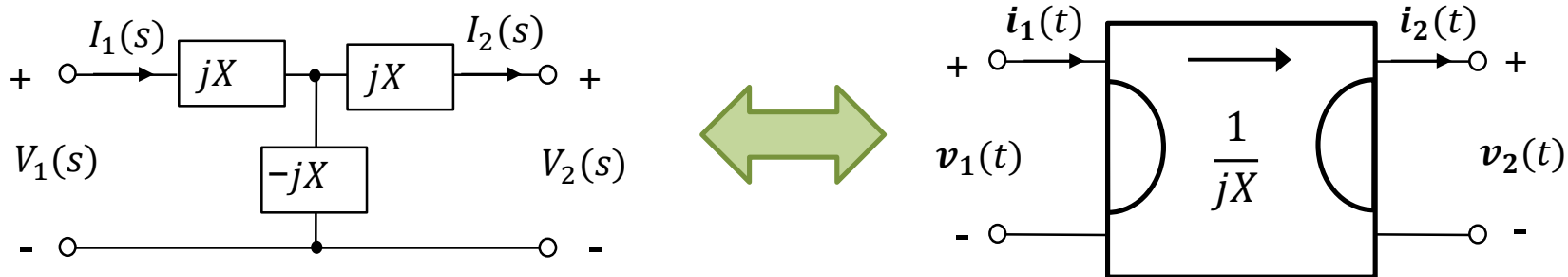
# Dynamic Gyrator Model for the Transient State IPT

- Proposed dynamic gyrator valid for complex time domain




$$I_2(s) = \mathbf{G}V_1(s) = V_1(s)/jX$$


$$I_1(s) = \mathbf{G}^*V_2(s) = -V_2(s)/jX$$

# Dynamic Phasor Circuit of an IPT

## □ T-Model in time domain

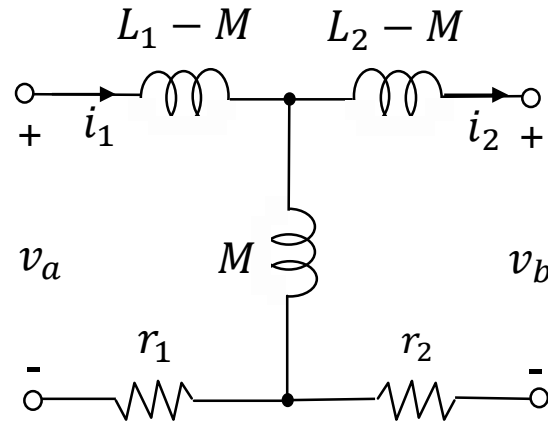


## □ Dynamic phasor circuit in s-domain

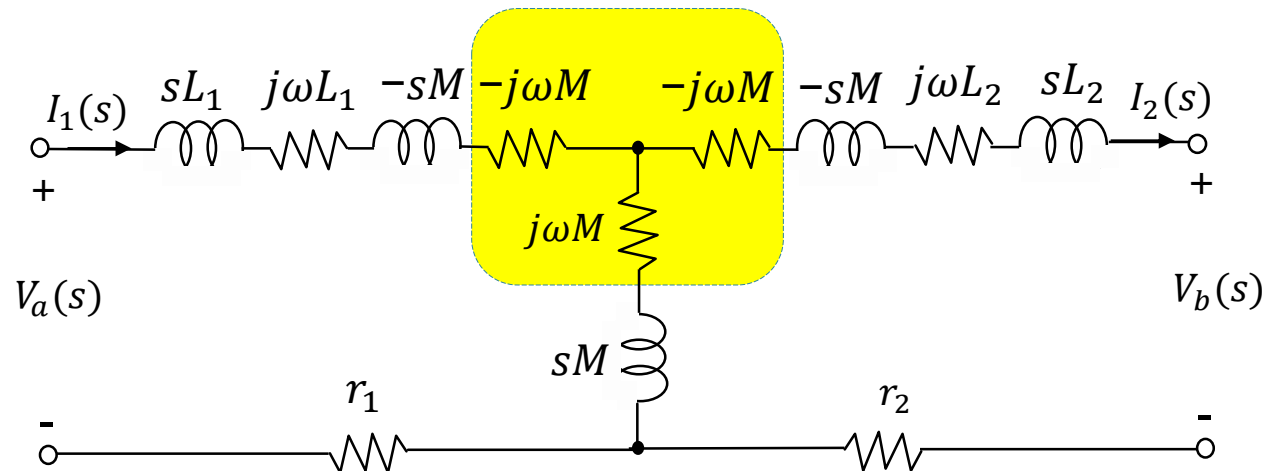

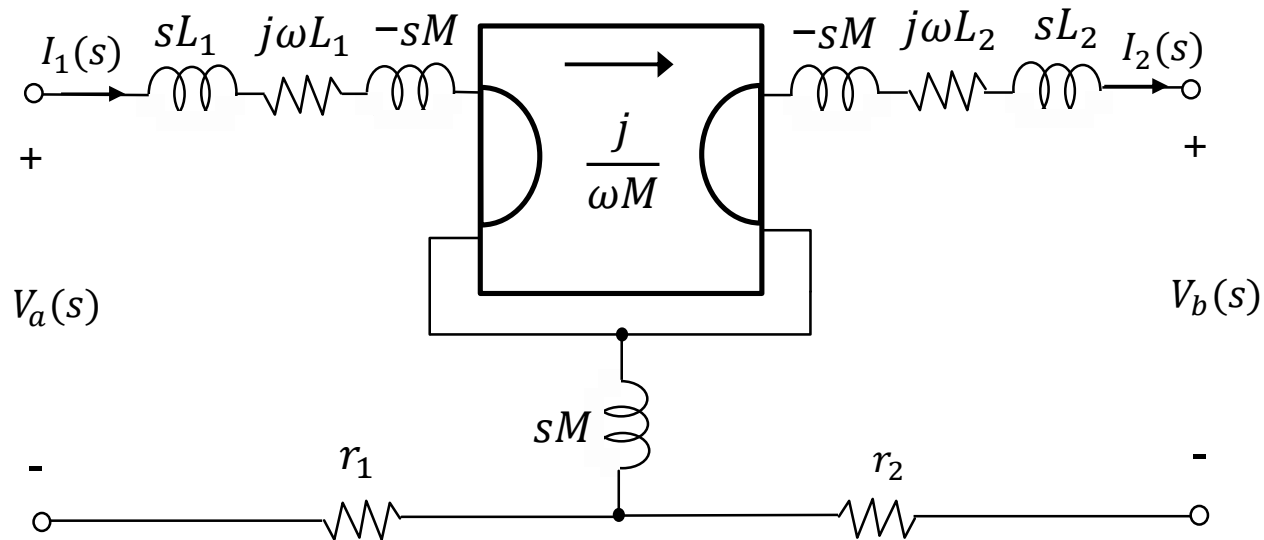
# Dynamic Phasor Circuit of an IPT

- Replacement with a dynamic gyrator in the dynamic phasor circuit



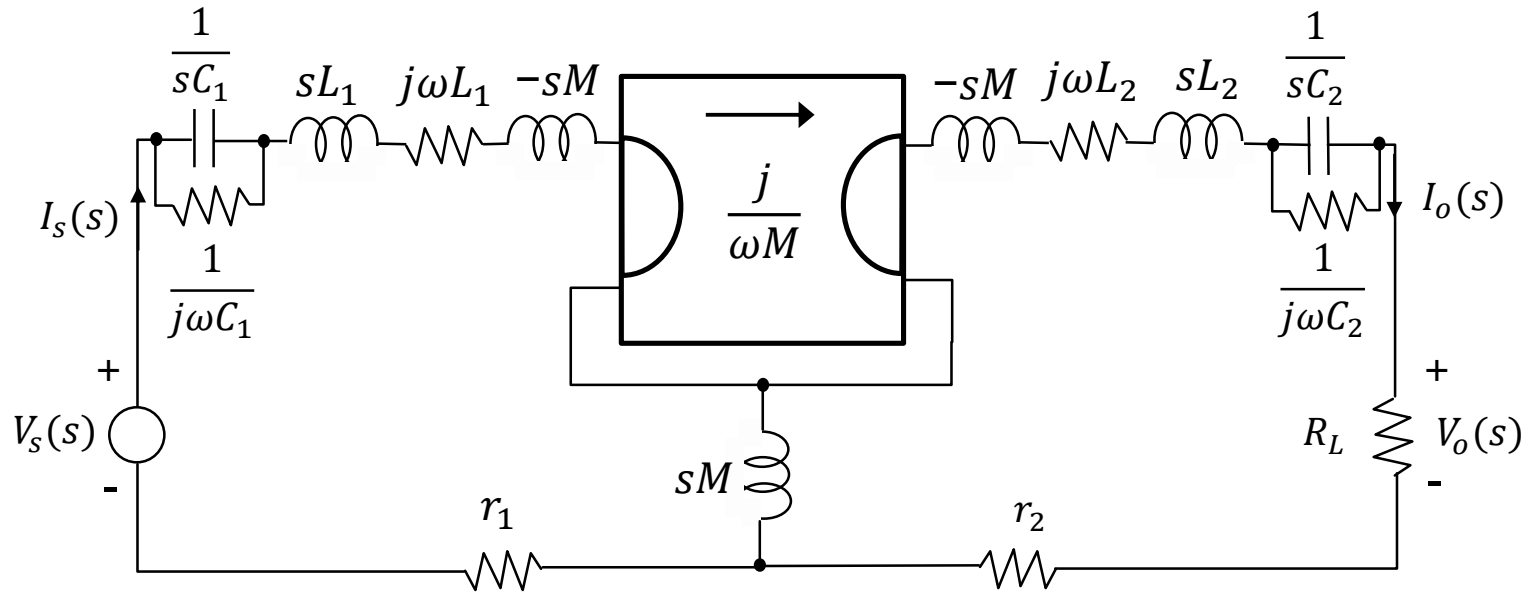
# Dynamic Gyrator-based IPT Circuit Analysis

- The dynamic phasor circuit of S-S IPT with a dynamic gyrator


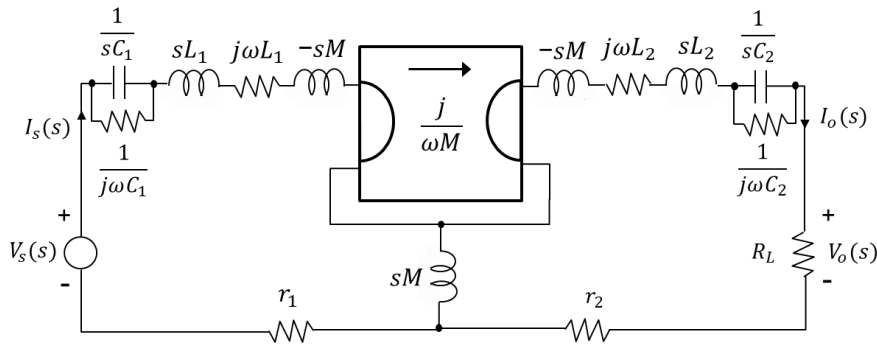
# Dynamic Gyrator-based IPT Circuit Analysis


□ A simplified dynamic phasor circuit in tuned case ( $\omega = \omega_r$ )



$$Z_s(s) \equiv \frac{1}{sC_1 + j\omega_r C_1} + sL_1 + j\omega_r L_1 = \frac{1}{j\omega_r C_1 \left(1 + \frac{s}{j\omega_r}\right)} + sL_1 + j\omega_r L_1 \cong$$

$$\frac{1}{j\omega_r C_1} \left(1 - \frac{s}{j\omega_r}\right) + sL_1 + j\omega_r L_1 = \frac{1}{j\omega_r C_1} + j\omega_r L_1 + \frac{s}{\omega_r^2 C_1} + sL_1 = 2sL_1,$$



$$\because |s| \ll \omega_r$$

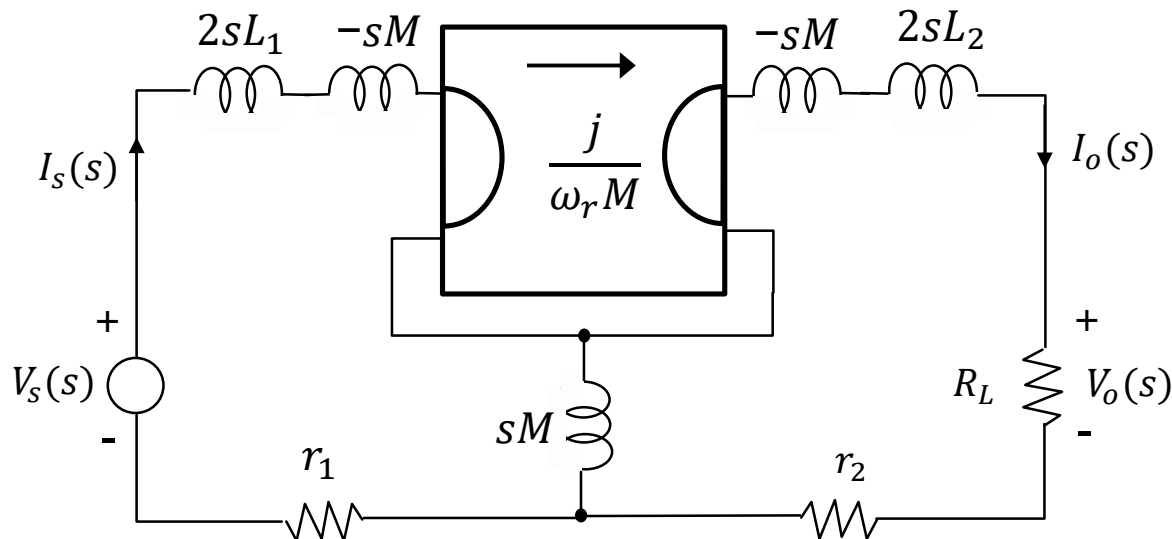




# Dynamic Gyrator-based IPT Circuit Analysis
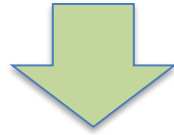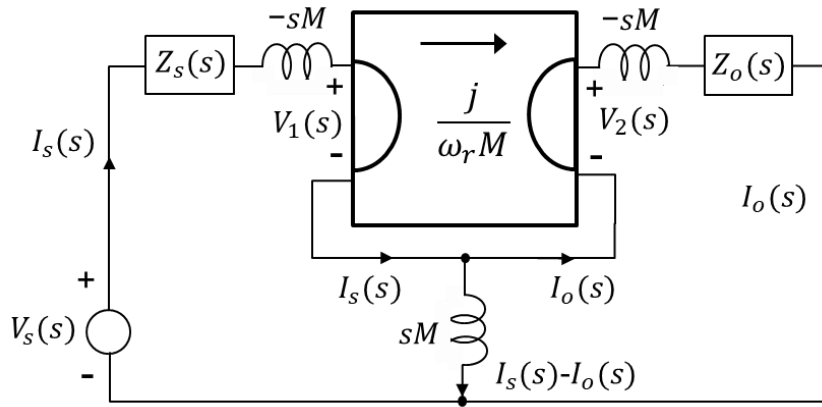
## □ Further simplified approximated circuit, eliminating s-terms



$$|s| \ll \omega_r$$

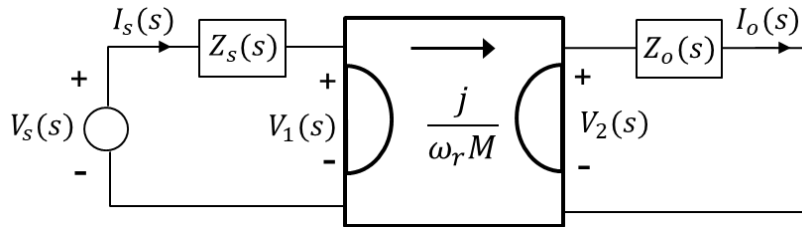

$$V_s(s) = Z_s(s)I_s(s) - sMI_s(s) + sM\{I_s(s) - I_o(s)\} + V_1(s)$$

$$= Z_s(s)I_s(s) - sMI_o(s) + V_1(s) = Z_s(s)I_s(s) + \frac{sMV_1(s)}{j\omega_r M} + V_1(s)$$

$$= Z_s(s)I_s(s) + V_1(s) \left(1 + \frac{s}{j\omega_r}\right) \cong Z_s(s)I_s(s) + V_1(s), \quad |s| \ll \omega_r$$


$$0 = Z_o(s)I_o(s) - sMI_o(s) + sM\{I_o(s) - I_s(s)\} - V_2(s)$$

$$= Z_o(s)I_o(s) - sMI_s(s) - V_2(s) = Z_o(s)I_o(s) - \frac{sMV_2(s)}{j\omega_r M} - V_2(s)$$

$$= Z_o(s)I_o(s) - V_2(s) \left(1 + \frac{s}{j\omega_r}\right) \cong Z_o(s)I_o(s) - V_2(s), \quad |s| \ll \omega_r$$


# Dynamic Gyrator-based IPT Circuit Analysis
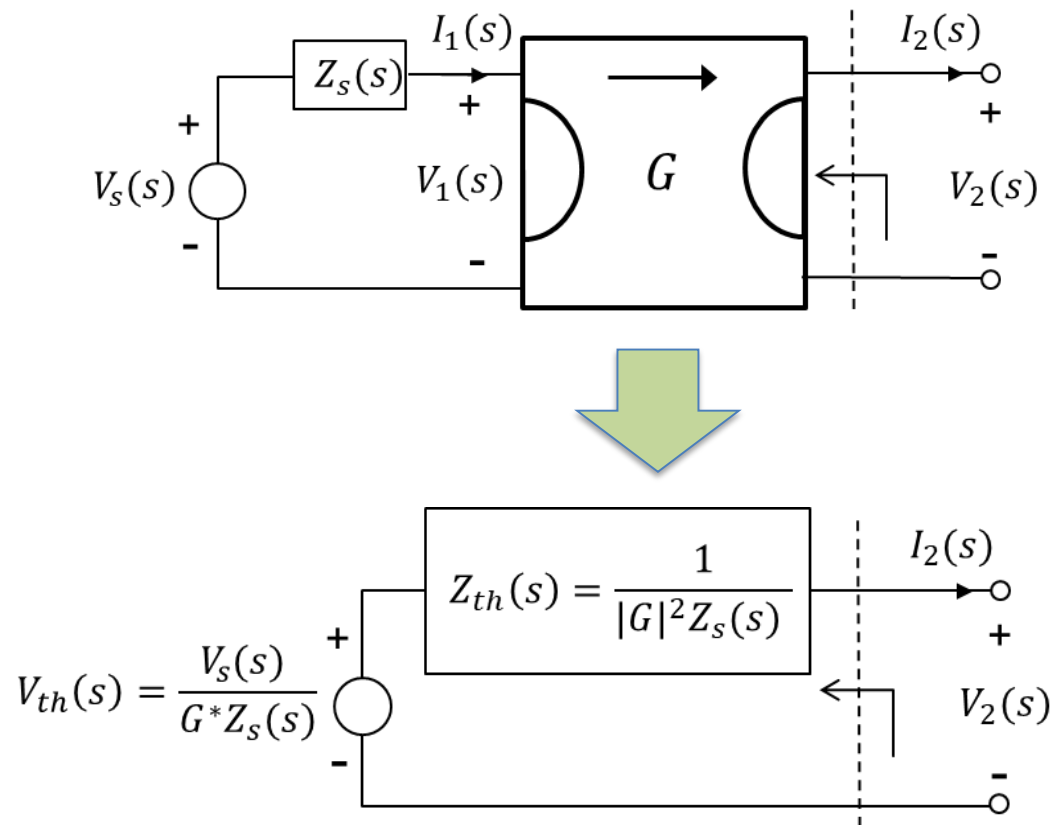
## □ Elimination of a dynamic gyrator from load side



# Dynamic Gyrator-based IPT Circuit Analysis


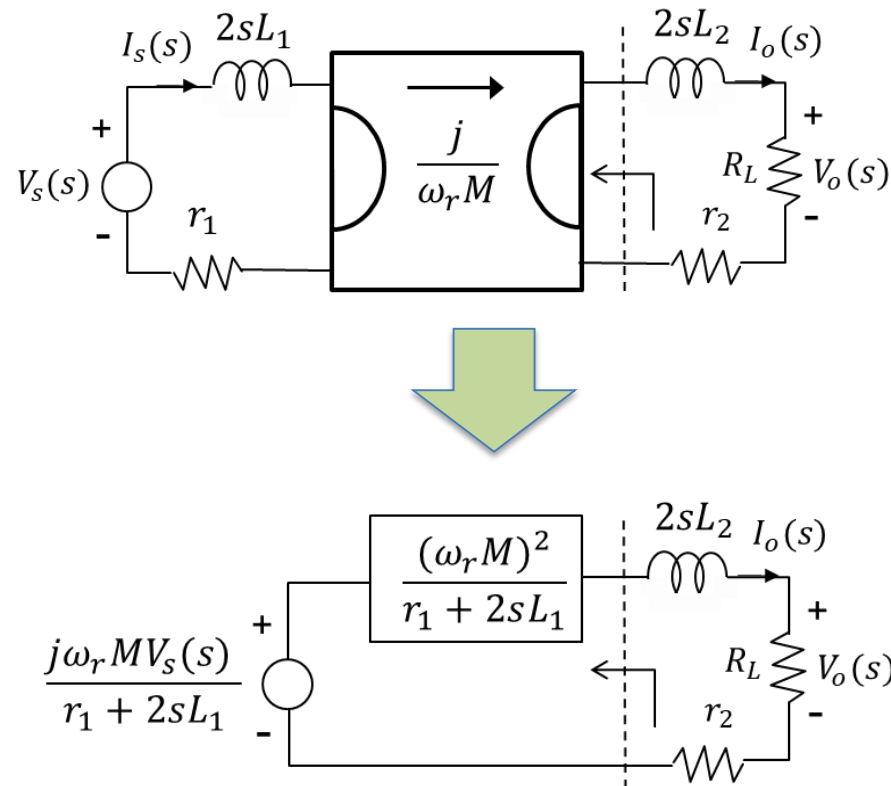
## □ Thevenin equivalent circuit of a dynamic gyrator



$$\begin{aligned}
 G_V(s) &\equiv \frac{V_o(s)}{V_s(s)} \\
 &= \frac{j\omega_r M}{r_1 + 2sL_1} \cdot \frac{R_L}{\frac{(\omega_r M)^2}{r_1 + 2sL_1} + r_2 + 2sL_2 + R_L} \\
 &= \frac{j\omega_r M R_L}{(\omega_r M)^2 + (r_1 + 2sL_1)(r_2 + R_L + 2sL_2)} = \\
 &= \frac{\frac{j\omega_r M R_L}{4L_1 L_2}}{s^2 + \left(\frac{r_1}{2L_1} + \frac{r_2 + R_L}{2L_2}\right)s + \frac{r_1 r_2 + r_1 R_L + (\omega_r M)^2}{4L_1 L_2}} \\
 &\rightarrow \zeta = \frac{\left(\sqrt{\frac{L_2}{L_1}} r_1 + \sqrt{\frac{L_1}{L_2}} R_2\right)}{2\sqrt{r_1 R_2 + (\omega_r M)^2}}
 \end{aligned}$$

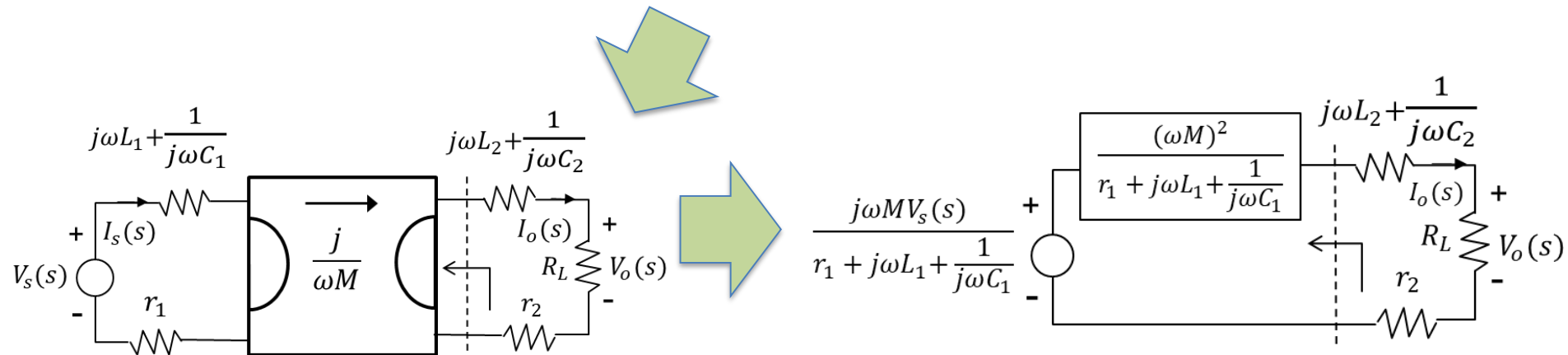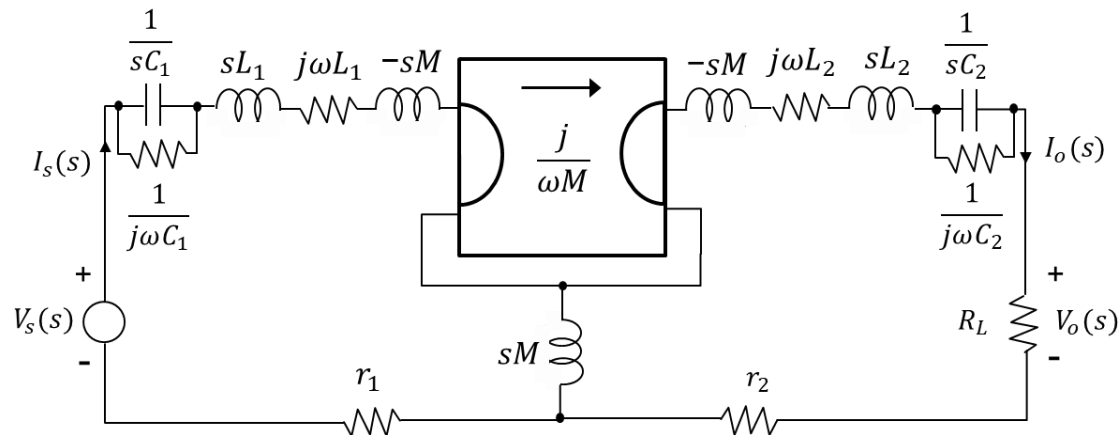
# Dynamic Gyrator-based IPT Circuit Analysis

- A simplified dynamic phasor circuit in mistuned case ( $\omega \neq \omega_r$ )


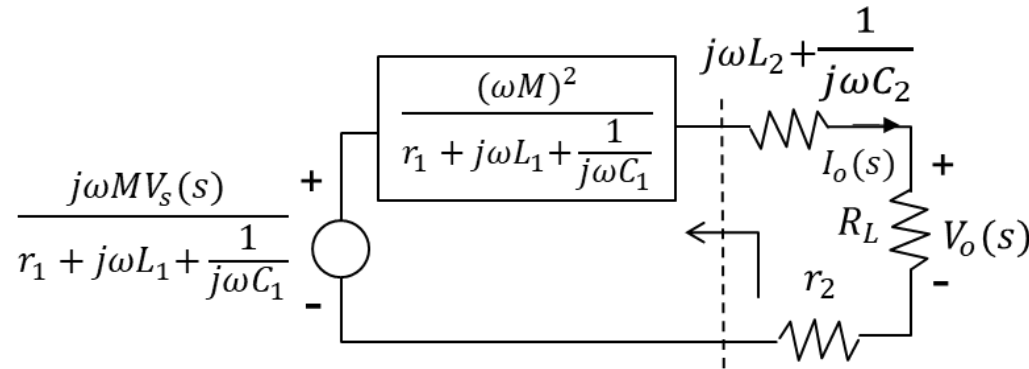
# Dynamic Gyrator-based IPT Circuit Analysis

- A simplified dynamic phasor circuit in mistuned case ( $\omega \neq \omega_r$ )




$$G_V(s) \equiv \frac{V_o(s)}{V_s(s)} = G_{V,dc}$$

$$\begin{aligned}
 &= \frac{j\omega M}{r_1 + j\omega L_1 + \frac{1}{j\omega C_1}} \cdot \frac{R_L}{\frac{(\omega M)^2}{r_1 + j\omega L_1 + \frac{1}{j\omega C_1}} + r_2 + j\omega L_2 + \frac{1}{j\omega C_2} + R_L} \\
 &= \frac{j\omega M R_L}{(\omega M)^2 + (r_1 + j\omega L_1 + \frac{1}{j\omega C_1})(r_2 + j\omega L_2 + \frac{1}{j\omega C_2} + R_L)}
 \end{aligned}$$

---

# III. Verifications by Simulation


# Simulation Conditions for Tuned Case

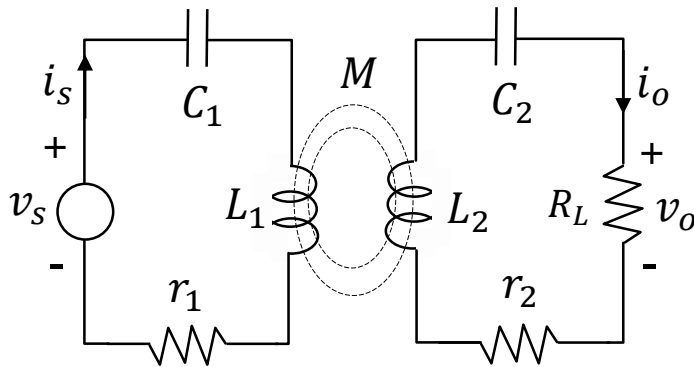

| No. | parameters | Values                   |
|-----|------------|--------------------------|
| 1   | $f_r$      | 50.3 (kHz)               |
| 2   | $L_1$      | 286.3 ( $\mu\text{H}$ )  |
| 3   | $L_2$      | 284.8 ( $\mu\text{H}$ )  |
| 4   | $M$        | 52.01 ( $\mu\text{H}$ )  |
| 5   | $C_1$      | 35.33 (nF)               |
| 6   | $C_2$      | 35.33 (nF)               |
| 7   | $r_1$      | 0.967 ( $\Omega$ )       |
| 8   | $r_2$      | 1.018 ( $\Omega$ )       |
| 9   | $R_L$      | 1.29~114.54 ( $\Omega$ ) |

# Simulation: $\zeta = 3$ , $R_L = 114.54\text{ohm}$


$$|s| \ll \omega_r$$

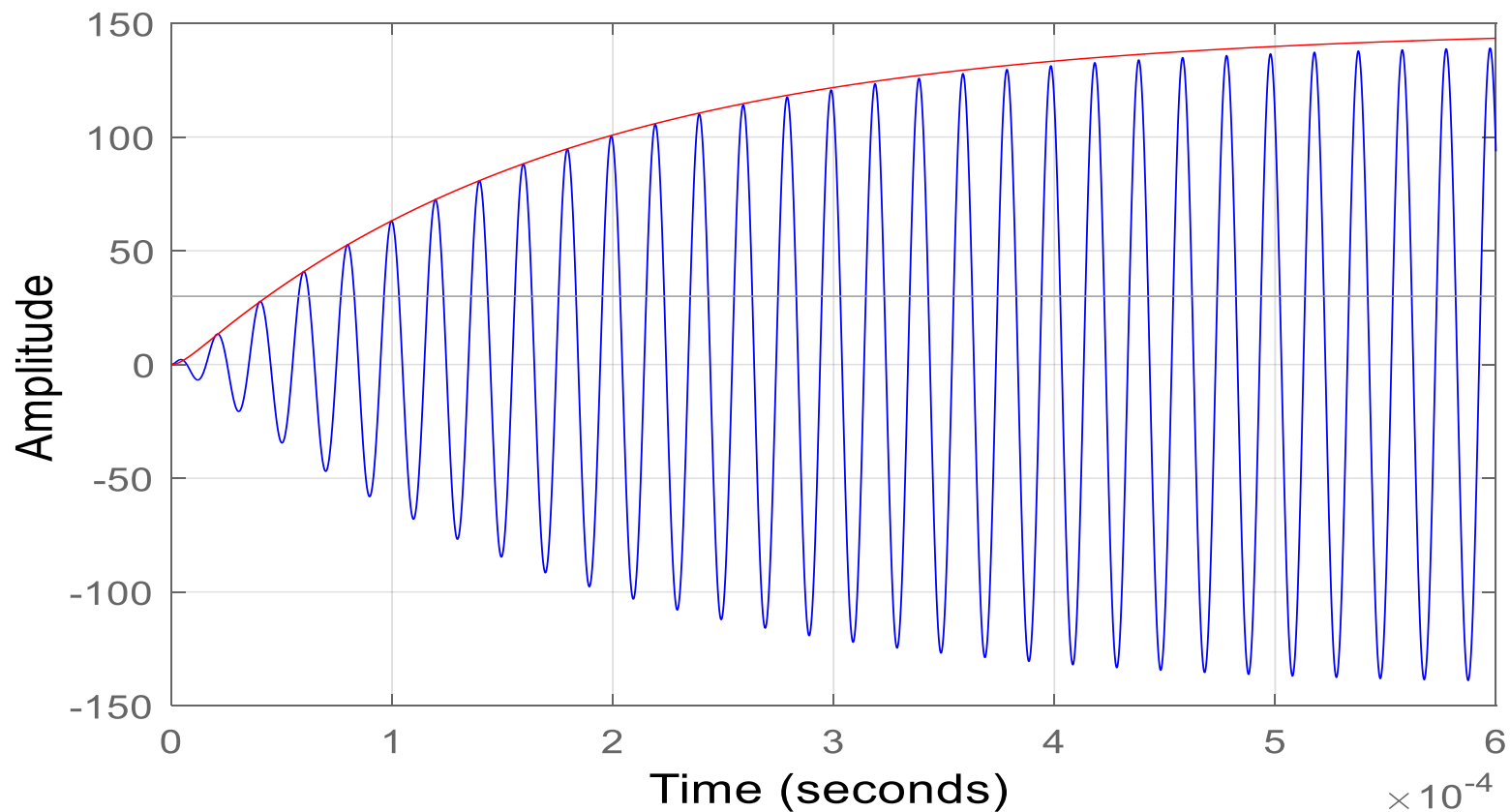




# Simulation: $\zeta = 1$ , $R_L = 32.55\text{ohm}$

$$|s| \ll \omega_r$$

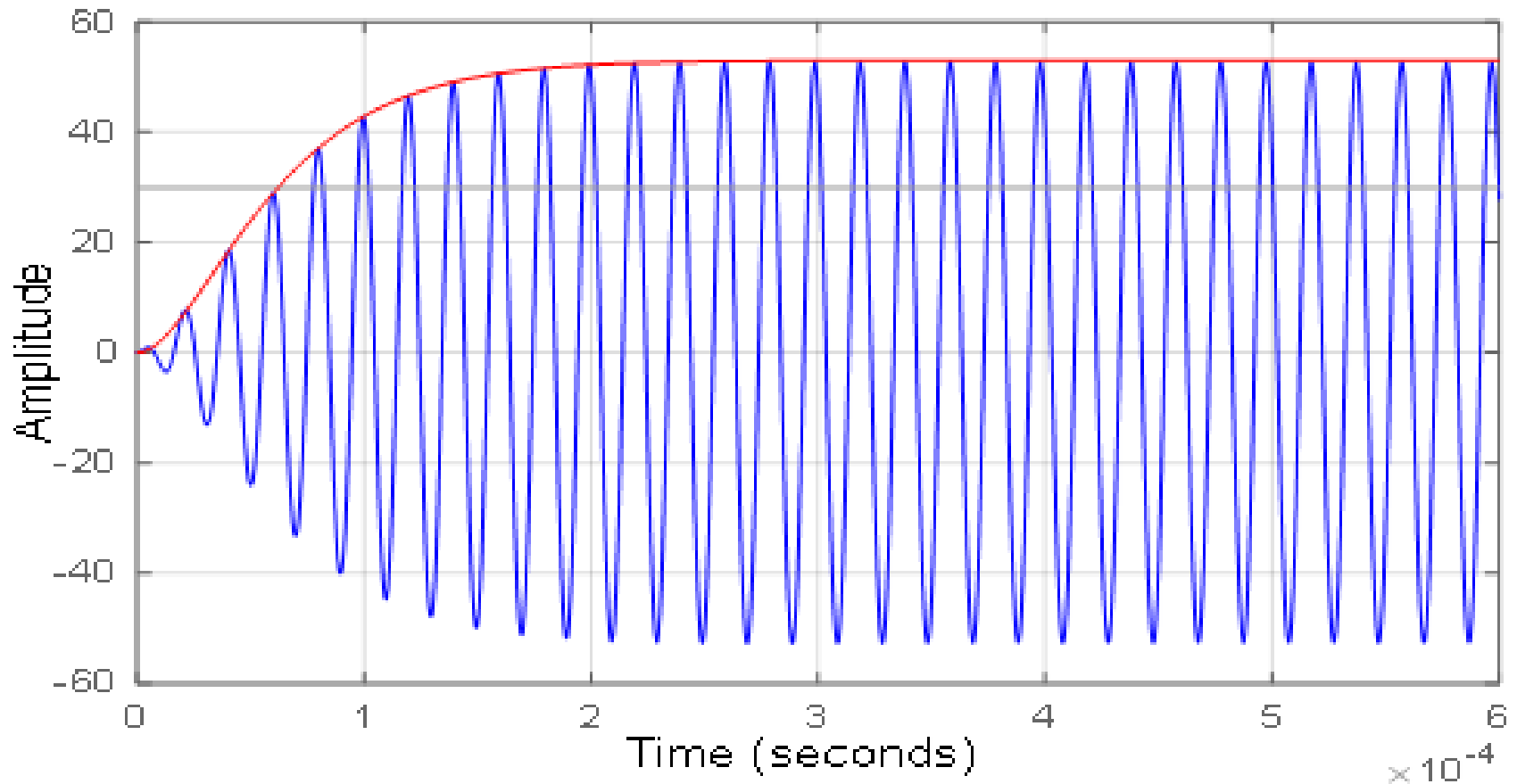


# Simulation: $\zeta = 0.3$ , $R_L = 7.95 \text{ ohm}$

$$|s| \ll \omega_r$$

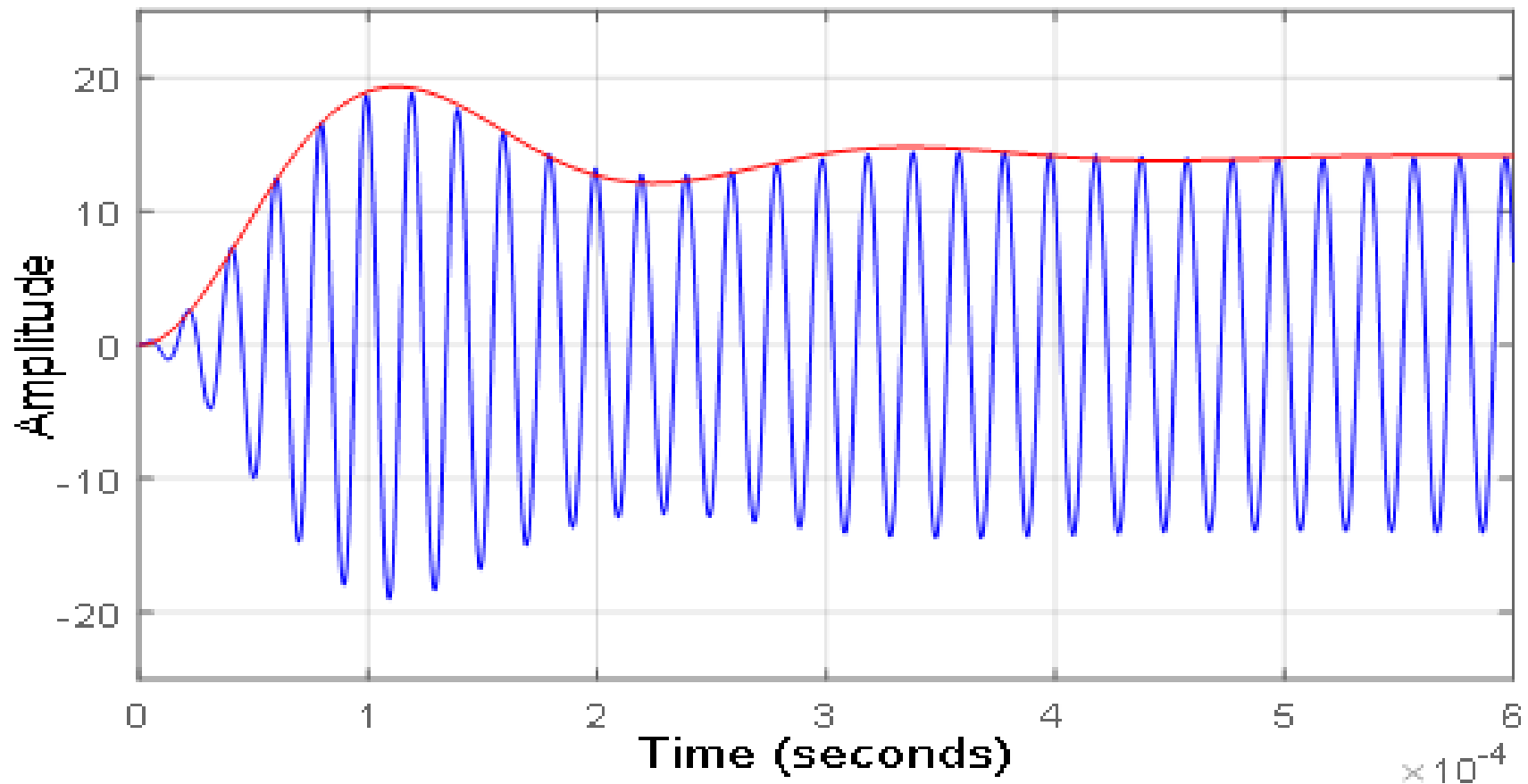

# Simulation: $\zeta = 0.1$ , $R_L = 1.29 \text{ ohm}$


$$|s| \ll \omega_r?$$

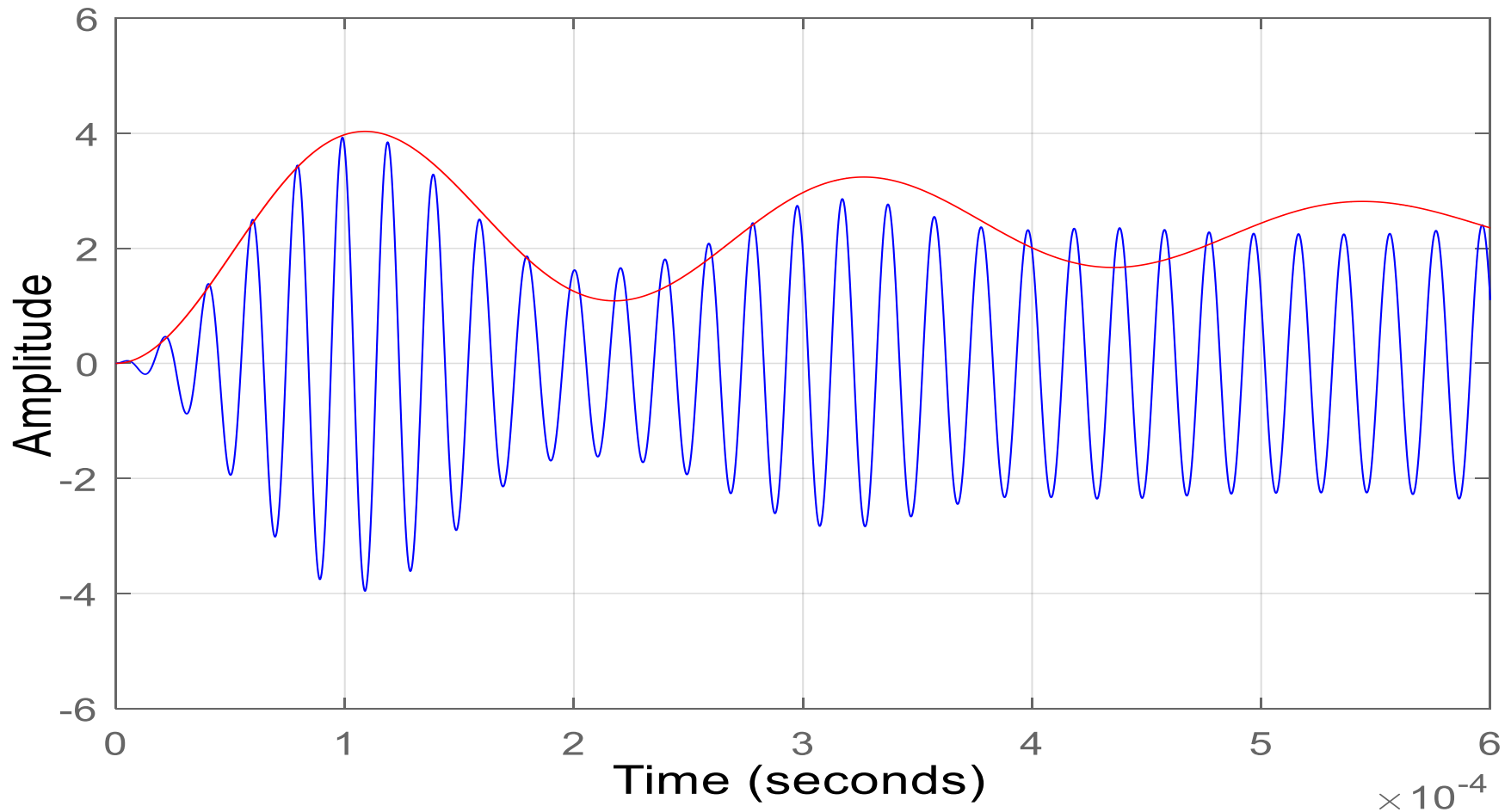


---

## IV. Experimental Verifications


# Experimental Kit

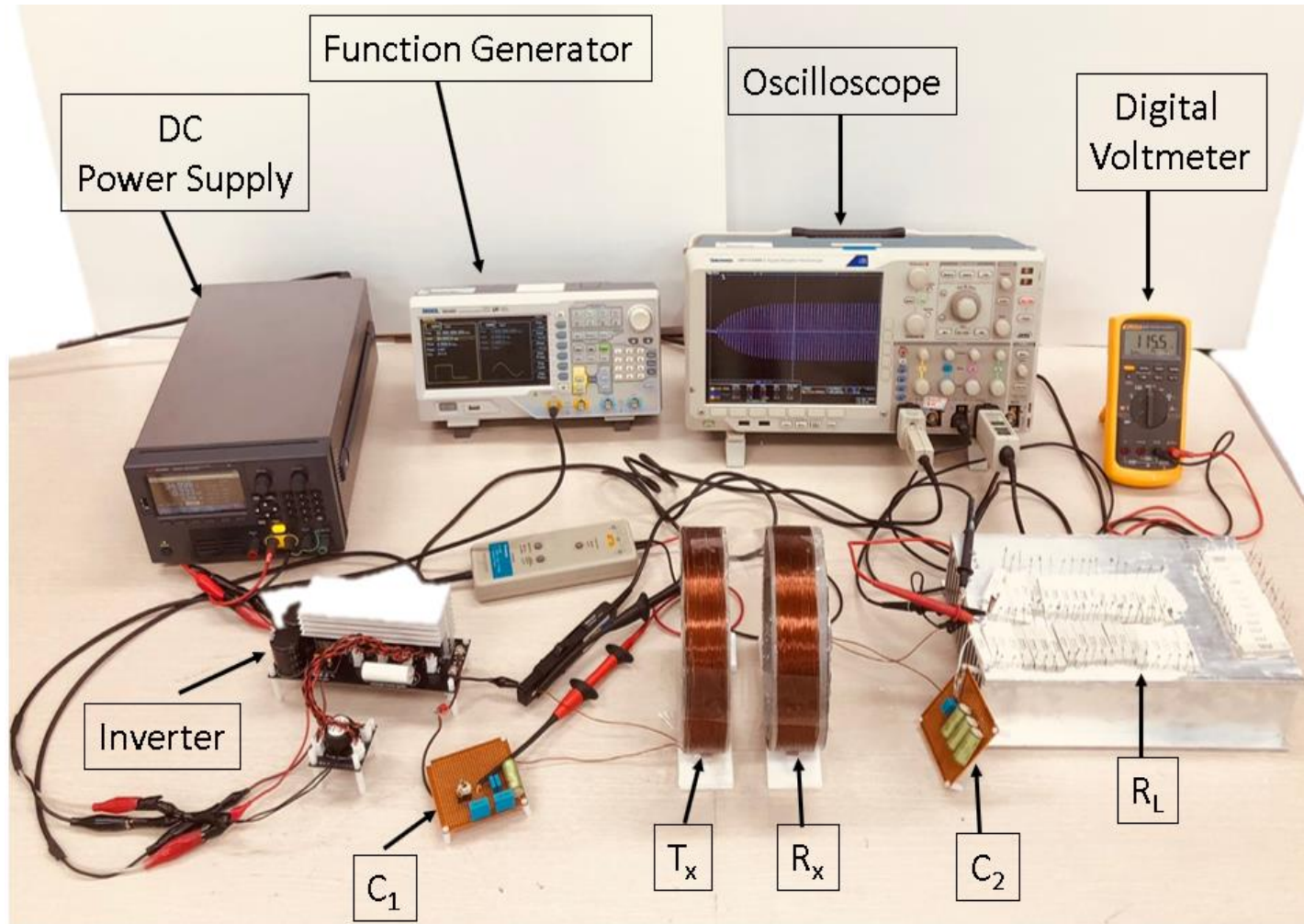

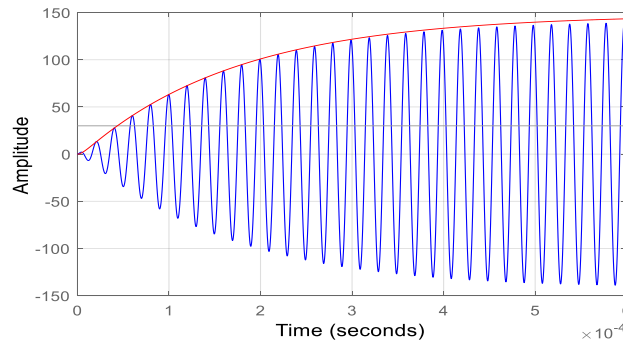
# Experiment: $\zeta = 3$ , $R_L = 114.54\text{ohm}$




$$|s| \ll \omega_r$$

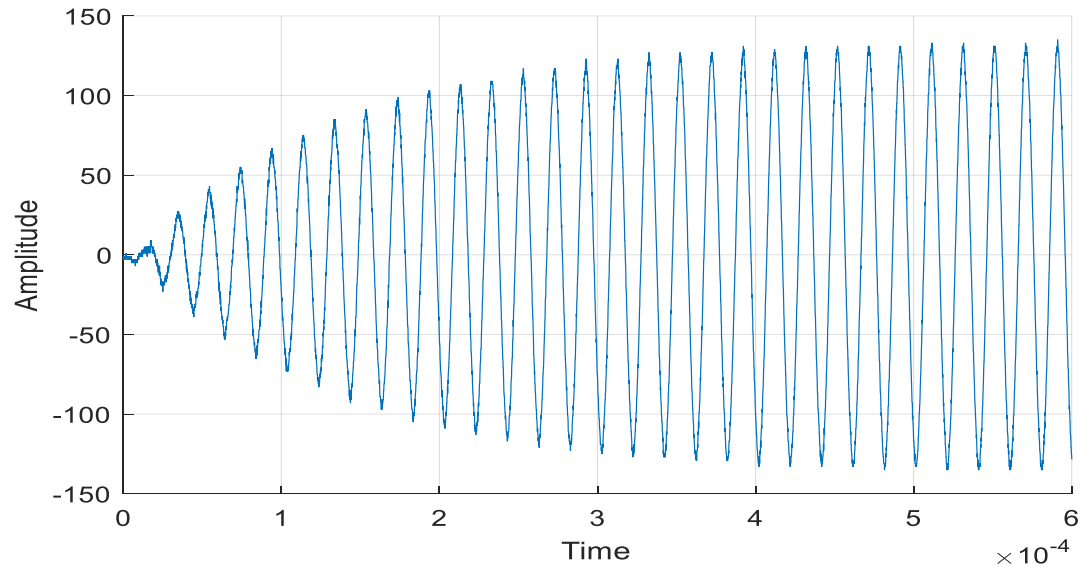

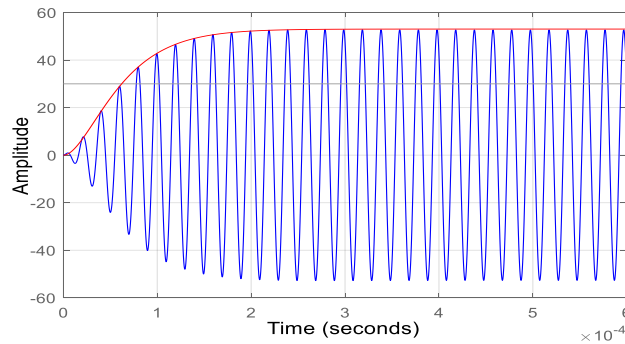
# Experiment: $\zeta = 1$ , $R_L = 32.55\text{ohm}$




$$|s| \ll \omega_r$$

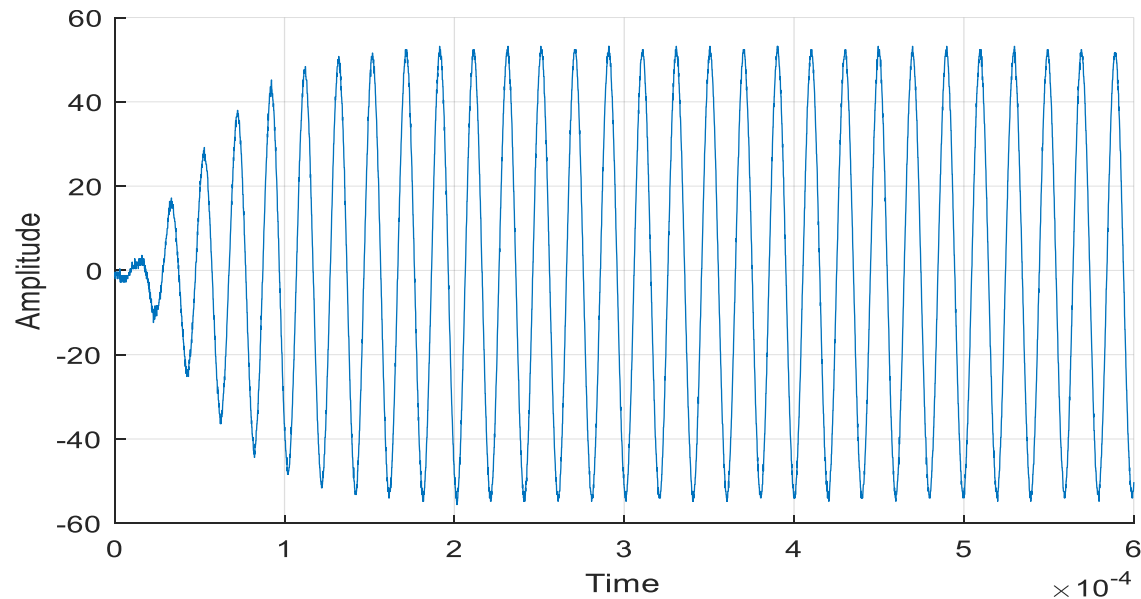
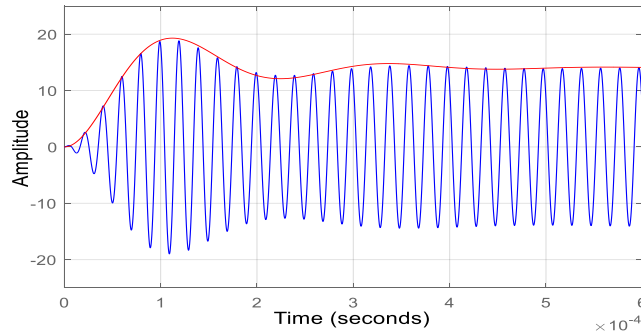
# Experiment: $\zeta = 0.3$ , $R_L = 7.95 \text{ ohm}$




$$|s| \ll \omega_r$$

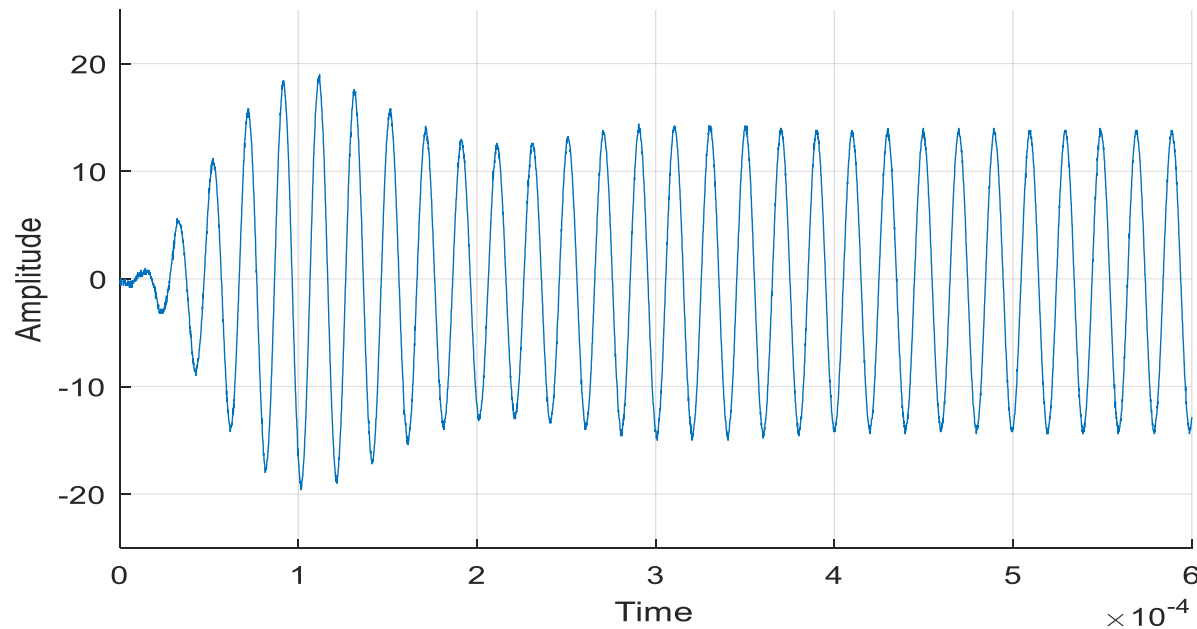



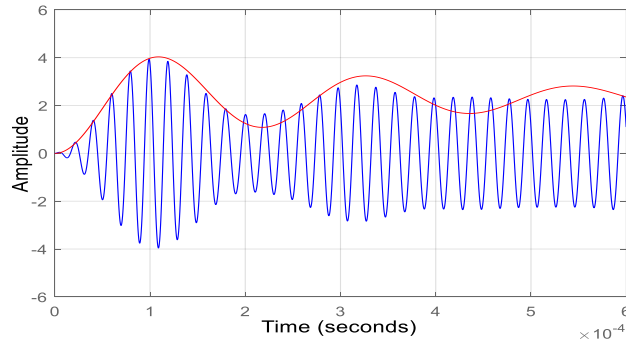
# Experiment: $\zeta = 0.1$ , $R_L = 1.29 \text{ ohm}$



$$|s| \ll \omega_r?$$

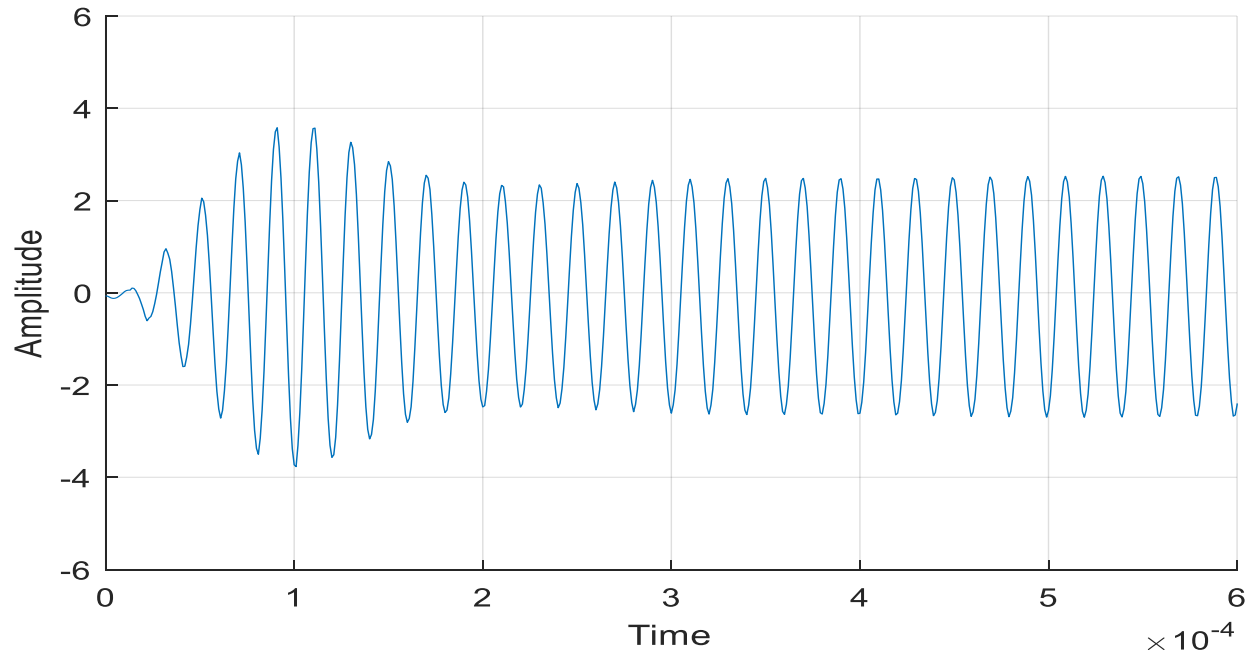


---

# V. Concluding Remark
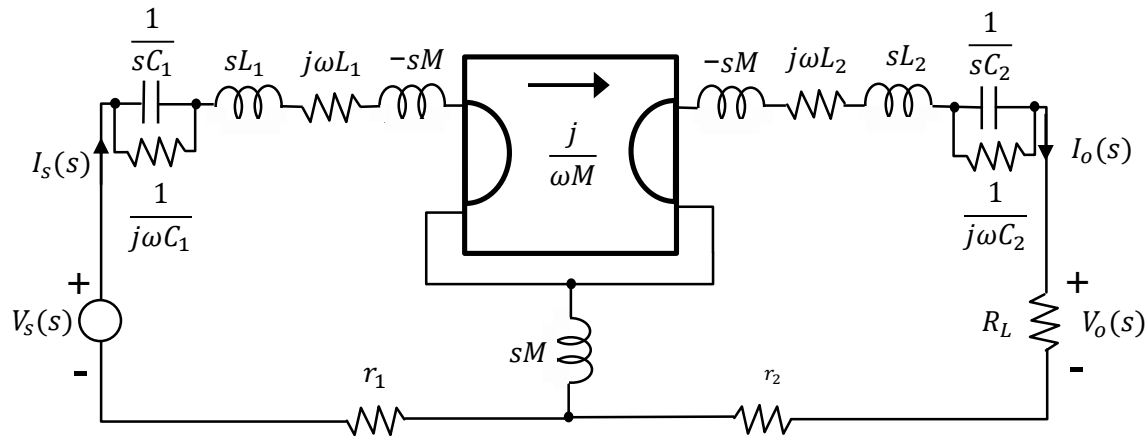
# IPT dynamics is simple & easy now!

- The 5<sup>th</sup> order IPT system becomes the 2<sup>nd</sup> order gyrator system



$$|s| \ll \omega_r$$

